

- DEUNIAAC REPORT -

Control Function & Microoperations Table

FETCH >>> T0: IR \leftarrow IM[PC]	
DECODE >>> T1: PC \leftarrow PC+1, Q \leftarrow IR (10), D0, D1...D15 \leftarrow Decode IR (9-6)	
DBL	D ₀ T ₃ :R _d \leftarrow shl RS ₁ , SC \leftarrow 0
DBT	D ₁ T ₃ :R _d \leftarrow shr RS ₁ , SC \leftarrow 0
ADD	D ₂ T ₃ :R _d \leftarrow RS ₁ + RS ₂ , SC \leftarrow 0
INC	D ₃ T ₃ :R _d \leftarrow RS ₁ + 1, SC \leftarrow 0
AND	D ₄ T ₃ :R _d \leftarrow RS ₁ \wedge RS ₂ , SC \leftarrow 0
NOT	D ₅ T ₃ : R _d \leftarrow RS ₁ ', SC \leftarrow 0
XOR	D ₆ T ₃ :R _d \leftarrow RS ₁ \oplus RS ₂ , SC \leftarrow 0
HLT	D ₇ T ₃ : SC _{en} \leftarrow 0
ST	D ₈ T ₃ Q': AR \leftarrow IR(3-0) D ₈ T ₄ Q': DM[AR] \leftarrow R _d , SC \leftarrow 0 D ₈ T ₃ Q: AR \leftarrow R _d D ₈ T ₄ Q: DM[AR] \leftarrow S ₁ S ₂ , SC \leftarrow 0
LD	D ₉ T ₃ Q': R _d \leftarrow S ₁ S ₂ , SC \leftarrow 0 D ₉ T ₃ Q: AR \leftarrow IR(3-0) D ₉ T ₄ Q: DM _{read} \leftarrow 1 D ₉ T ₅ Q: D ₉ T ₆ Q: R _d \leftarrow DM[AR], SC \leftarrow 0
IO	D ₁₀ T ₃ Q': OutR \leftarrow RS ₁ , SC \leftarrow 0 D ₁₀ T ₃ Q: R _d \leftarrow InpR, SC \leftarrow 0
TSF	D ₁₁ T ₃ : R _d \leftarrow RS ₁ , SC \leftarrow 0
JMP	D ₁₂ T ₃ Q': PC \leftarrow IR (4-0), SC \leftarrow 0 D ₁₂ T ₃ QV: PC \leftarrow IR (4-0), SC \leftarrow 0
CAL	D ₁₃ T ₃ : SM[SP] \leftarrow PC D ₁₃ T ₄ : SP \leftarrow SP + 1, PC \leftarrow IR (4-0), SC \leftarrow 0
RET	D ₁₄ T ₃ : SP \leftarrow SP - 1 D ₁₄ T ₄ : SM _{read} \leftarrow 1 D ₁₄ T ₅ : D ₁₄ T ₆ : PC \leftarrow SM [SP], SC \leftarrow 0
JMR	D ₁₅ T ₃ : PC \leftarrow PC + S ₁ S ₂ , SC \leftarrow 0

Write Selection Table (4 Bits)

Sel_write[2..0]	SELECTION
000	ALU_out
001	Rd (R0-R1-R2)
010	S1S2
011	DM[AR]
100	S1 (R0-R1-R2)
101	INPR

I used the output "sel_write[2..0]" for selection of writeable data in the bus system. A MUX can control the data. This data can be load into *AR*, *Rd*, *DM[AR]*, *OUTR*.

Program Counter Selection Table (5 Bits)

Sel_PC[1..0]	SELECTION
00	SM[SP]
01	PC
10	Address
11	PC+offset

I used the output "sel_PC[1..0]" for selection of writeable data for program control in the bus system. A MUX can control the data. This data can be load into *PC*, *SM[SP]*.

Load Selection Table (in BUS)

Signal Name	Load into
LD_AR	AR
LD_PC	PC
LD_Rd	Rd
LD_IR	IR
DMW	Data Memory[AR]
SMW	Stack Memory[SP]
In	INPR
Out	OUTR

Using these signals I can insert writable data into fields.

Assembly Code

	ORG I 0	;Origin of instruction memory
0	LD R0, @A	;Load operand from address A to R0
I1	LD R1, @C	;Load counter from location C to R1
I2	INC R2, R1	;Increment R1 (counter) and store to R2
I3	JMP 8, Q	;If v= 1 jump to HLT and finish the program
I4	TSF R1, R2	;Transfer counter value to R1.
I5	ADD R2, R0, R1	;Add R0 and R1, store in R2
I6	TSF R0, R2	;Transfer R2 (sum) to R0
I7	JMR -5	;Jump to beginning of loop
I8	HLT	;Halt computer
	ORG D 0	;Origin of data segment
D0	A: DEC 2	;Decimal value 2
D1	C: DEC 12	;Decimal value 12

Assembly Code

INSTRUCTION NUMBER	INSTRUCTION NAME	BINARY
I0	LD	1 1001 00 0000
I1	LD	1 1001 01 0001
I2	INC	X 0011 10 01 XX
I3	JMP (to I8)	1 1100 X 01000
I4	TSF	X 1011 01 10 XX
I5	ADD	X 0010 10 00 11
I6	TSF	X 1011 00 10 XX
I7	JMR (-6)	X 1111 XX 1110
I8	HLT	X 0111 XX XX XX

Assembly to binary

Since I initially increased the PC during Decode-Fetch in the Control unit, I took the situation under control by making -6 instead of -5 in the JMR process.

Loops

Loop 0

<u>NUMBER</u>	<u>INSTRUCTION</u>	<u>CHANGE</u>
I0	LD	R0
I1	LD	R1
I2	INC	R2
I3	JMP (to I8)	X
I4	TSF	R1
I5	ADD	R2
I6	TSF	R0
I7	JMR (-6)	X

Loop 1

<u>NUMBER</u>	<u>INSTRUCTION</u>	<u>CHANGE</u>
I2	INC	R2
I3	JMP (to I8)	X
I4	TSF	R1
I5	ADD	R2
I6	TSF	R0
I7	JMR (-6)	X


Loop 2

<u>NUMBER</u>	<u>INSTRUCTION</u>	<u>CHANGE</u>
I2	INC	R2
I3	JMP (to I8)	X
I4	TSF	R1
I5	ADD	R2
I6	TSF	R0
I7	JMR (-6)	X

Loop 3

<u>NUMBER</u>	<u>INSTRUCTION</u>	<u>CHANGE</u>
I2	INC	R2
I3	JMP (to I8)	X
I8	HLT	Halt comp.

Design and Improvements

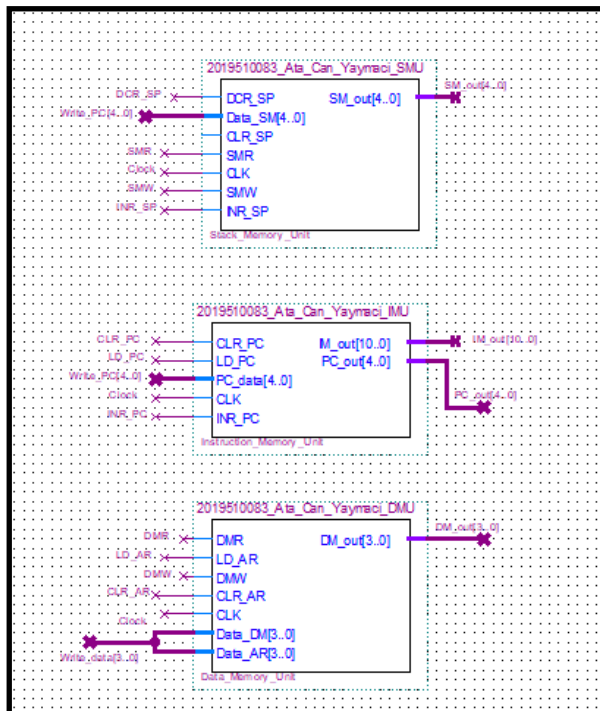


Memory Units


SMU is “Stack Memory unit” with a Stack Pointer and a Stack Memory(5x16).

IMU is “Instruction Memory unit” with a Program Counter and an Instruction Memory(11x32).

 
DMU is “Data Memory unit” with an Address Register and a Data Memory(4x16).




Control unit

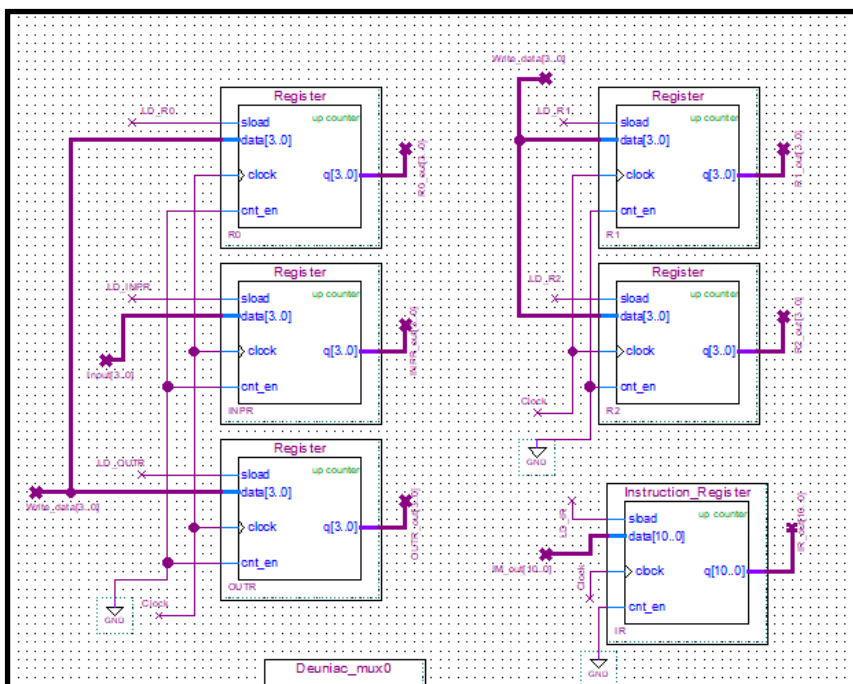

Registers (R0/R1/R2/INPR/OUTR/IR)

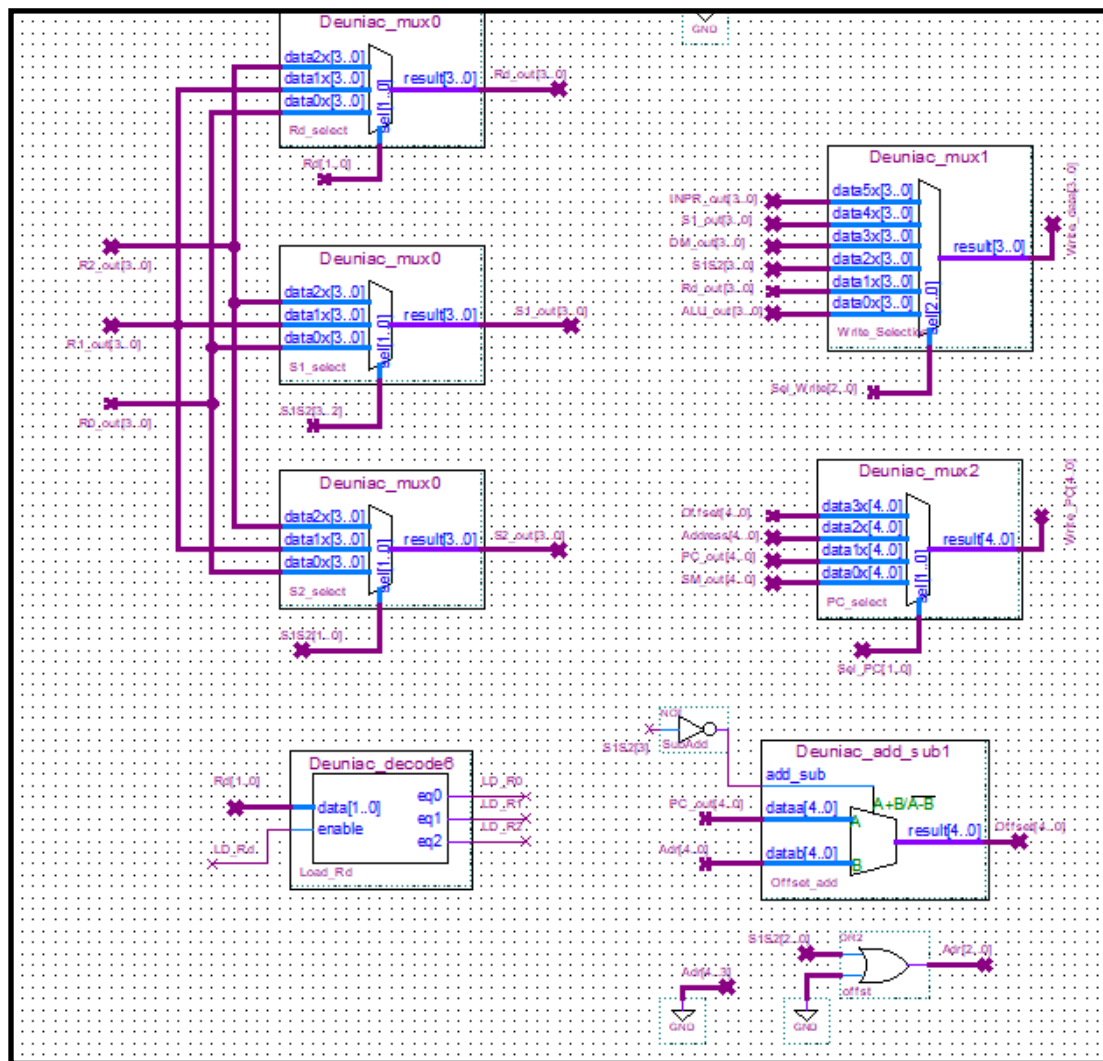



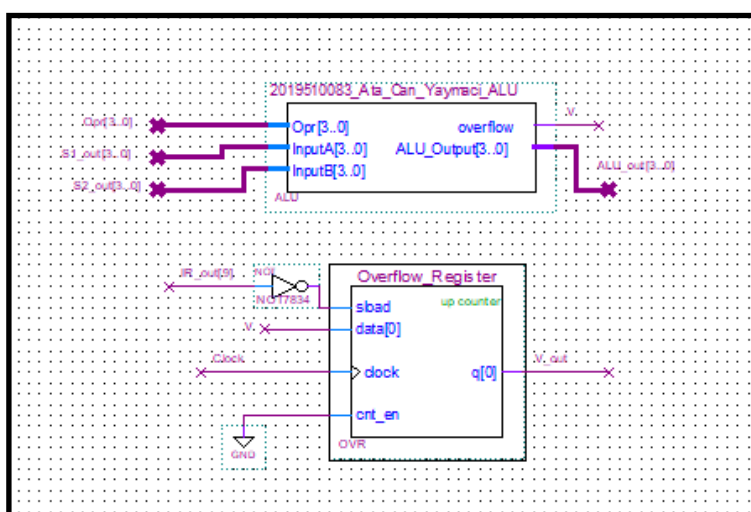










 
 






Selections and an offset calculator



ALU and overflow register

Since overflows are not stored correctly during checks (JMP), I saved the overflow with a register.

Waveform

	Name	Value at 0 ps
	> Input	B 0000
	Clock	B 0
	> SC	B 000
	> IR_out	B 000000000000
	> OUTF_out	B 0000
	> PC_out	B 00000
	Q	B 0
	V_out	B 0
	> S1S2	B 0000
	> Rd	B 00
	> Write_data	B 0000
	> Write_PC	B 00000
	LD_AR	B 0
	LD_Rd	B 0
	LD_IR	B 1
	LD_PC	B 0
	> R0_out	B 0000
	> R1_out	B 0000
	> R2_out	B 0000
	> DM_out	B 00000
	> SM_out	B 00000

Input: Input for INPR

Clock: Clock for system

SC: System counter (T0/T1/T2/T3/T4/T5/T6)

IR_out: Instruction register

OUTR_out: Output register

PC_out: Program counter

Q: Most significant bit in instruction

S1S2: IR(3..0)

Rd: IR(5..4) selects R0/R1/R2

Write_data: Selection for writeable data (with a 4bit mux)

Write_PC: Selection for writeable data (with a 5bit mux)

LD_AR: Load signal for AR

LD_IR: Load signal for IR

LD_PC: Load signal for PC

R0_out: R0 register

R1_out: R1 register

R2_out: R2 register

DM_out: DM[AR] (Data memory)

SM_out: SM[SP] (Stack memory)

Waveform headers